Contents: Active Filters

- Introduction
- Butterworth 1, 2rd order Filters
 (Low, High)
- Narrow, Wide Band Pass Filters
- Narrow, Wide Band Reject Filter
- All Pass Filter

Linear Ic Apps

PASS

in High Pass filter in All pass filter LOW PASS FILTER HILLMO SUBORY Gam A litter broduces 0.7 STOP BAND BAND BAND PASS FILTER:

Gam

0.7

Based on operation,

Types of filters:

Cotoff Frequency:

It is defined as the frequency at which the gain is:

- in 1/12 of maximum
- (in 70% of maximum
- (11) 3dB lesser than the maximum (m dB)

The filter maximum gain is unity.

Differences between the active filter and passive, filter:

- ch A Passive filters are designed by R.L.C whereas it active filters are designed by R.C and any active element like op-amp. con transistor.
- in External supply is not needed in passive filter whereat is used in active filter because the active element has to be operated.
- ciù) Roll-Off (Slope of the curve between pass, band and stop band) is less in passive filter and it is more in active filter (ideal filter, roll-off is infinite)
- in Passive filter will not produce amplification in poss band but active filter produces.

BUTTER WORTH FILTER

PASS TO STOP BAND

RIPPLES DONOT EXIST


tg: Low pass filter

CHEBYSHEV FILTER

PASS fo STOD F

RIPPLES EXIST
IN STOP BAND AND
PASS BAND

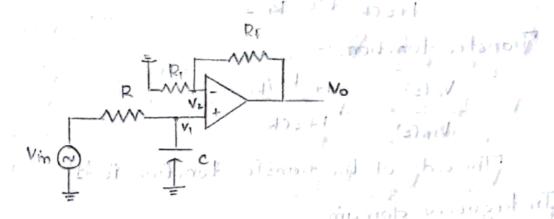BUTTERWORTH 1st ORDER LOW PASS FILTER (ACTIVE):



The cricuit is in negative feedback.

$$V_1 = V_2$$
.

and $V_1=V_2=0$ because currents entering into op-amp input terminals is zero.

Applying the modal analysis at non-inverting terminal of op-amp in Laplace domain,

$$\frac{V_{1}-V\dot{m}(s)}{R} + \frac{V_{1}+O}{1/c_{6}} + O = 0$$

$$\frac{V_{1}-V\dot{m}(s)}{R} = -cs \left[V_{1}\right] - \frac{V_{1}}{R}$$

$$V_{1}\left[1+scR\right] = R. \frac{V\dot{m}(s)}{R}$$

$$V_{1} = \frac{V\dot{m}(s)}{1+scR}$$

Apply the nodal analysis at inverting terminal, (of op-amp)

$$\frac{V_2 - O}{R_1} + \frac{V_2 - V_0}{R_f} + O = O$$

$$\frac{V_0(s)}{1 + R_f/R_1} = V_2$$

$$V_0(s) = V_2 \left[1 + \frac{R_f/R_1}{R_f/R_1} \right]^{\frac{1}{2} + \frac{1}{2} + \frac{1}{2}} \left[\frac{(ah)}{ah} \frac{(ah)}{ah} \right]^{\frac{1}{2} + \frac{1}{2} + \frac{1}{2}} \left[\frac{(ah)}{ah} \frac{(ah)} \frac{(ah)}{ah} \frac{(ah)}{ah} \frac{(ah)}{ah} \frac{(ah)}{ah} \frac{(ah)}{ah}$$

which the characters and

Transfer function.


The order of the transfer function is 1

In frequency domain,

If we apply de signal as input (f=0) Vin Vin 1+0 monost RF > 1 in pro 10 in

Input is an ac signal with higher frequency f= 00, $\frac{V_0}{V_{im}} = 0$

So, frequency response,

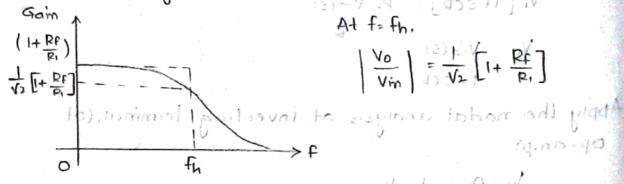

At f= fh,

$$\left|\frac{V_0}{V_m}\right| = \frac{1}{V_2} \left[1 + \frac{R_f}{R_i}\right]$$

0 + 0 + 0 - V + 0 + 0 + V so, at f=fh.

$$\frac{V_0(f_h)}{V_{1\dot{n}}(f_h)} = \frac{1+Rf/R_1}{1+j(2\pi f_h)Rc}$$

$$\frac{V_0(f_h)}{V_{\dot{m}}(f_h)} = \frac{1+Rf/R_1}{\sqrt{1+(2\pi f_h)Rc}}$$


$$\frac{1}{\sqrt{2}} \left[1 + \frac{Rf}{R_1} \right] = \frac{1 + \frac{Rf}{P_1}}{\sqrt{1 + (2\pi f_h Rc)^2}}$$

$$1 + 2\pi f_h Rc = 2$$

$$\frac{1}{\int_{h}} \frac{1}{2\pi Rc}$$

22-09-15

Ist order Butterworth High Pass filter:

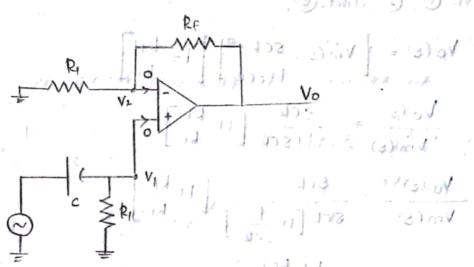

for negative feedback

Applying Nodal analysis at the mon-investing terminal in Laplace domain.

$$\frac{V_{1}-V\dot{m}(s)}{R \, l/sc} + \frac{V_{1}-O}{R} + O = 0$$

$$V_{1} \left[sc+\dot{p}\right] - V\dot{m}(s) \cdot sc = 0$$

$$V_{1} \left[\frac{sc+l}{R}\right] - V\dot{m}(s) \cdot sc = 0$$

$$V_{1} \left[\frac{sc+l}{R}\right] - V\dot{m}(s) \cdot sc = 0$$

$$V_{1} \left[\frac{sc+l}{R}\right] - V\dot{m}(s) \cdot \frac{sc}{l+sc} \rightarrow 0$$

Applying nodal analysis at investing terminal in Taplace

$$\frac{V_2 - O}{R_1} + \frac{V_2 - V_0(s)}{R_f} + O = O$$

$$V_2 \left[\frac{1}{R_1} + \frac{1}{R_f} \right] - \frac{V_0(s)}{R_f} = O$$

$$V_2 \left[\frac{R_1 + R_f}{R_1 R_f} \right] = \frac{V_0(s)}{R_1 R_f}$$

$$V_0(s) = V_2 \left[\frac{1}{R_1} + \frac{R_f}{R_1} \right] \rightarrow 3$$

$$V_0(s) = \left[V_m(s) \cdot \frac{scR}{1 + scR} \right] \left[\frac{1}{R_1} + \frac{R_f}{R_1} \right]$$

$$\frac{V_0(s)}{V_m(s)} = \frac{scR}{1 + scR} \left[\frac{1}{R_1} + \frac{R_f}{R_1} \right]$$

$$\frac{V_{\text{in}}(s)}{V_{\text{in}}(s)} = \frac{\text{SeR}}{\text{SeR}} \left[1 + \frac{RF}{R_{1}} \right]$$

$$= \frac{1 + \frac{RF}{R_{1}}}{1 + \frac{1}{3} \text{cR}} \left[1 + \frac{RF}{R_{1}} \right]$$

$$= \frac{1 + \frac{RF}{R_{1}}}{1 + \frac{1}{3} \text{cR}} \left[1 + \frac{RF}{R_{1}} \right]$$

midletiolApollitiRF/RPM, and to regione labored profile

$$\frac{V_{o}(s)}{V_{m}(s)} = \frac{A_{o}}{1 + 1/s_{cR}}$$

In the frequency domain, $\frac{Vo(f)}{V\dot{m}(f)} = \frac{-A_0}{1 + \frac{1}{i2\pi fRc}}$

It for Vin is an Ac signal with high frequency. Gom a collict and to by an assembly of An V2 At f= fe 1/2 | Vo | 1= Ao mil of miles and and man $\left|\frac{V_{0}(f)}{V_{in}(f)}\right| = \frac{A_{0}}{\sqrt{1+\left(\frac{1}{2nfRc}\right)^{2}}}$ $f = f. \left(\text{Cut off frequency}\right)$ At f= fi (cot off frequency), 1 . No = No = VI+(2x fe RC)

fe = 1 01x ax pel 6210.

The maximum gain of the filter is Ao = 1+ Rf and the eutoff frequency is fl= 1

· Design a butterworth Ist order low pass filter with a maximum gain of 5, with a cutoff frequency loktz and plot the frequency response

The maximum gain of the filter is,

$$A = 1 + \frac{Rf}{R_1}$$

$$5 = 1 + \frac{Rf}{R_1}$$

 $kt/b' = 4 \Rightarrow kt = 4k'$

Let Ri = 1 ka, then Rf = 4 ka

from the expression for time coloff frequency,

(A) of

. (granumant 185 HD) of File


27 ×10 ×1000

Let c= o.luf,

$$= \frac{0.0159}{0.1 \times 10^6 \times 10^3} = 159 \text{ kp.} \times 10^3$$

= 159A

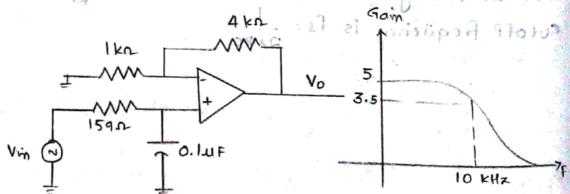and have the the state of the to the mon rome of



· Design a butterworth first order active high pass filter, with a maximum gain 9, cutoff frequency 1 kHz. The maximum gain of the filter is, -A0 = 1+ RF d= 1+ Bt Let R= 1 ka, then Rf= 8 ks from the expression for cutoff frequency. fe = 1 KHz = = 0.1591×10 Let c= o.l uf, = 1591.54 & = 1.59 K2

teate Hast

· Design butterworth active low pass and high pass filters with maximum gain 20 dB and with cutoff frequency lookyz and plot the frequency response

$$H = 1 + \frac{kt}{kt}$$

$$20\log\left[1+\frac{Rt}{Rt}\right] = 20$$


$$\frac{Rf}{R_1} = 9$$

Let Ri= 1 ka, Rf = 9 ka


-As the cutoff frequency is 100 kHz,

$$R = \frac{1}{2\pi \times 10^5 \times C}$$

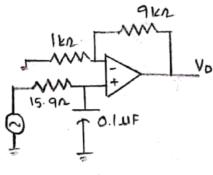
$$R = \frac{1}{2\pi \times 10^{5} \times 0.1 \times 10^{6}}$$
= 15.90



LOW PASS

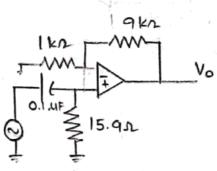

HIGH PASS

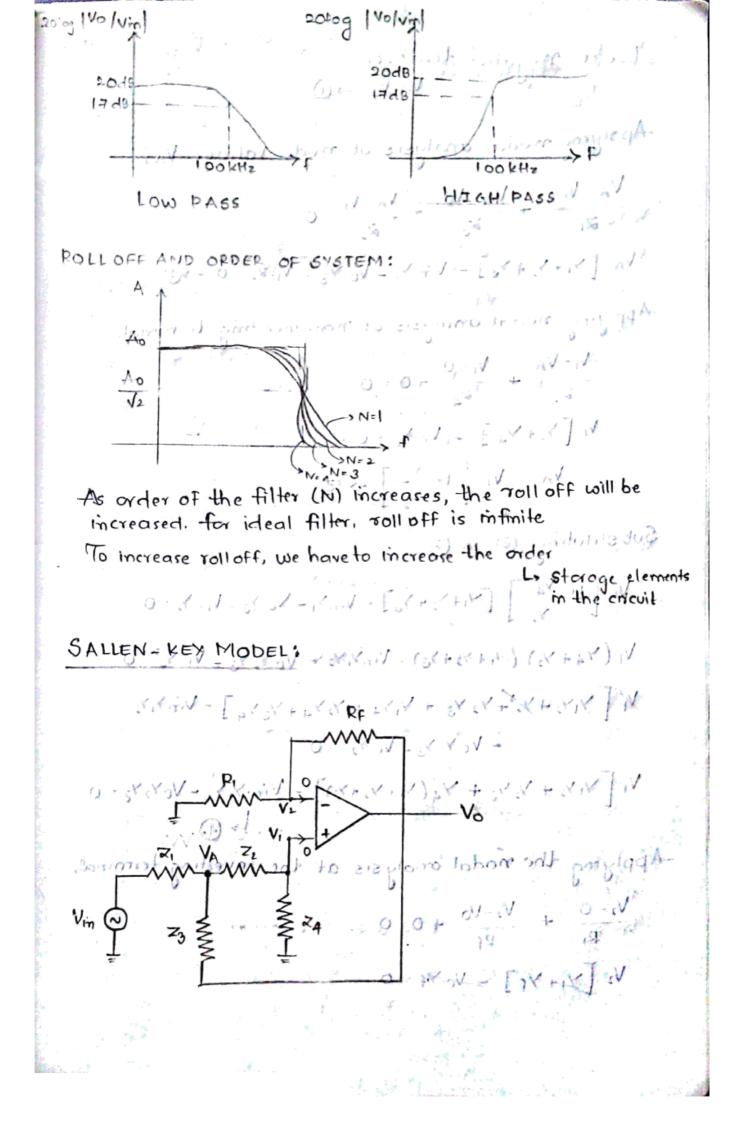

Applying modal analysis at mode voltage VA,

$$\frac{V_{A}-V_{\dot{m}}}{z_{1}}+\frac{V_{A}-V_{0}}{z_{3}}+\frac{V_{A}-V_{1}}{z_{2}}=0$$

Applying nodal analysis at non-inverting terminal,

$$\frac{V_1 - V_A}{\approx_2} + \frac{V_1 - 0}{\approx_4} + 0 = 0$$

Substituting 3 in 3,

$$Y \left[Y_1 Y_2 + Y_2 Y_3 + Y_1 Y_4 + Y_2 Y_4 + Y_3 Y_4 \right] - V_m Y_1 Y_2$$

$$- V_0 Y_2 Y_3 - V_1 Y_2^2 = 0$$

Applying the modal analysis at the investing terminal,

$$\frac{V_{2}-0}{R_{1}} + \frac{V_{2}-V_{0}}{R_{f}} + 0 = 0$$

$$V_{2} \left[\frac{R_{1} + R_{f}}{R_{1}R_{f}} \right] = \frac{V_{0}}{R_{f}}$$

$$V_{0} = V_{2} \left[\left(\frac{R_{f}}{R_{1}} \right) \right]$$

$$= V_{2} \left[A_{0} \right]$$


$$-A_{0} = \frac{V_{0}}{V_{2}} \Rightarrow V_{2} = \frac{V_{0}}{A_{0}} \Rightarrow (5)$$

$$Substituting (5) \text{ in (4)},$$

$$\frac{V_{0}}{A_{0}} \left[\frac{Y_{1}Y_{2} + Y_{2}Y_{3} + Y_{4} (Y_{1} + Y_{2} + Y_{3})}{A_{0}} \right] = V_{in} \frac{Y_{1}Y_{2} + V_{0} Y_{2} Y_{3}}{Y_{1}Y_{2} + (1 - A_{0})Y_{2}Y_{3} + Y_{4} (Y_{1} + Y_{2} + Y_{3})} = V_{in} \frac{Y_{1}Y_{2}}{Y_{1}Y_{2}} A_{0}$$

$$\frac{V_{0}}{V_{in}} = \frac{Y_{1}Y_{2} + (1 - A_{0})Y_{2}Y_{3} + Y_{4} (Y_{1} + Y_{2} + Y_{3})}{Y_{1}Y_{2} + (1 - A_{0})Y_{2}Y_{3} + Y_{4} (Y_{1} + Y_{2} + Y_{3})}$$
Butterworth first order Active Low Pass filter!:

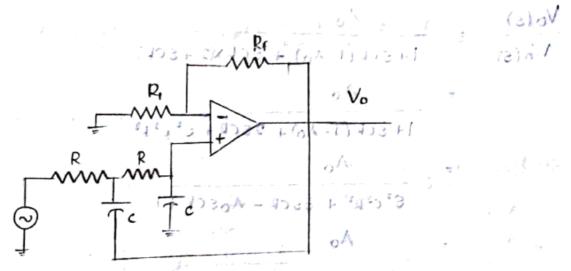Butterworth first order Active Low Pass filter:



By companing the above chicuit with Sallen key model,

$$Z_{1} = R$$

$$Z_{2} = R$$

$$Z_{3} = 1/sc$$

$$Z_{4} = 1/sc$$

$$Z_{5} = R$$

$$Z_{6} = R$$

$$Z_{7} =$$

1 (04 &)) STRE (& 40) =1

$$\frac{V_{1} = 1/R}{V_{2} = 1/R}$$

$$\frac{V_{3} = sc}{V_{4} = sc}$$

$$\frac{V_{n}(s)}{V_{n}(s)} = \frac{\frac{1}{R^{2}} + \frac{sc}{R}(1-A_{0}) + \frac{sc}{R} + \frac{sc}{R}c^{2}}{\frac{1}{R^{2}} + \frac{sc}{R}(1-A_{0}) + \frac{sc}{R}c^{2}} + \frac{sc}{R}c^{2}}$$

$$= \frac{A_{0}}{R^{2}}$$

$$\frac{1}{R^{2}} + \frac{sc}{R}(1-A_{0}) + \frac{sc}{R}c^{2} + \frac{sc}{R}c^{2}$$

$$= \frac{A_{0}}{R^{2}}$$


$$\frac{1}{R^{2}} + \frac{sc}{R}(1-A_{0}) + \frac{sc}{R}c^{2}(\frac{2}{R}+sc)$$

$$\frac{1}{R^{2}} + \frac{sc}{R^{2}} + \frac{sc}{R^{2}}c^{2}$$

$$\frac{A_{0}}{R^{2}} + \frac{sc}{R^{2}}c^{2}$$

$$\frac{A_{0$$

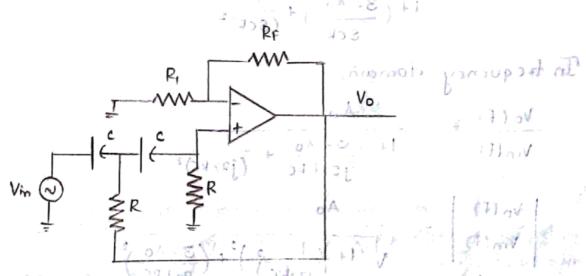BUTTERWORTH LIND ORDER ACTIVE HIGH PASS FILTER



Comparing the above with the Sallen key model,

\$\overline{\pi_1} = 1/sc \overline{\pi_3} = R

(sa 5) + (sans) + /

Due to negative feedback,

$$V_1 = V_2$$

$$V_{in}(s) = (sc)^{2} + (1-A_{0}) \frac{sc}{R} + \frac{1}{R} (sc+sc+\frac{1}{R})$$

$$=$$
 $(sc)^2 A_0$

$$= \frac{A_0}{1 + \left(\frac{3 - A_0}{SCR}\right) + \frac{1}{\left(SCR\right)^2}}$$

In frequency domain,

$$\frac{V_{0}(f)}{V_{m}(f)} = \frac{A_{0}}{12\pi FRC} + \frac{1}{(j2\pi RC)^{2}}$$

$$\frac{|V_0(f)|}{|V_m(f)|} = \frac{A_0}{\sqrt{\left(\frac{1}{2\pi Rc}\right)^2 + \left(\frac{3-A_0}{2\pi FRC}\right)^2}}$$

The quantity, the = 1

$$= \sqrt{1+\left(\frac{1}{-\ln Rc}\right)+\left(\frac{3-Ao}{2}\right)^2}$$

$$=\frac{A_0}{1-\int (3-A_0)} + \frac{1}{(2\pi RC)^2}$$

$$=\frac{V_0(f)}{V_m(f)} = \frac{A_0}{\left(1-\frac{1}{(2\pi RC)^2}\right)^2 + \left(\frac{3-A_0}{2\pi fRC}\right)^2}$$

$$\left[\text{et } f_2 = \frac{1}{2\pi RC} + \frac{1}{(2\pi RC)^2}\right]^2 + \left[\frac{3-A_0}{2\pi fRC}\right]^2$$


$$V_m(f) = \frac{A_0}{V_m(f)} = \frac{A_0}{V_m(f)} + \frac{1}{(2\pi RC)^2} + \frac{1}{(2\pi RC)^2}$$

$$\frac{V_0(f)}{V_m(f)} = \frac{A_0}{V_m(f)} + \frac{1}{(2\pi RC)^2} + \frac{1}{(2\pi RC)^2}$$

$$\frac{V_0(f)}{V_m(f)} = \frac{A_0}{V_m(f)} + \frac{1}{(2\pi RC)^2} + \frac{1}{(2\pi RC)^2} + \frac{1}{(2\pi RC)^2}$$

$$\frac{V_0(f)}{V_m(f)} = \frac{A_0}{V_m(f)} + \frac{1}{(2\pi RC)^2} + \frac$$

ALL PASS FILTER!

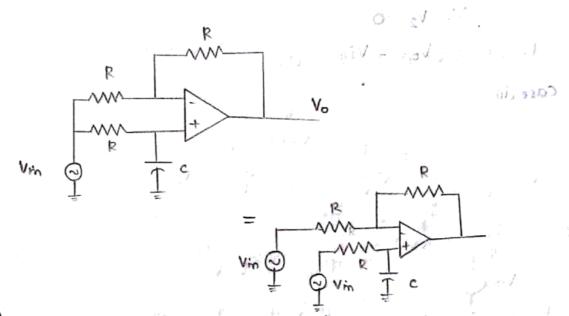

According to the super position the orem,

In an ITI system consisting of more one source, the


total response at one element is equal to algebraic sum

of individual responses.

Two cases are obtained,

in Output Vo,

in Output Vo,

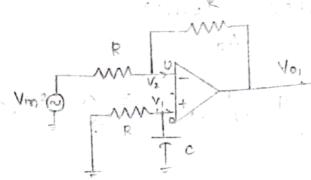

for negative feed bock, VI=V2


Since $V_1=0$, $V_1=V_2=0$

Applying notal analysis at investing terminal.

$$\frac{V_2 - V_{100}}{R} + \frac{V_2 - V_{01}}{R} = 0$$

$$V_2 = 0$$

Case cii)

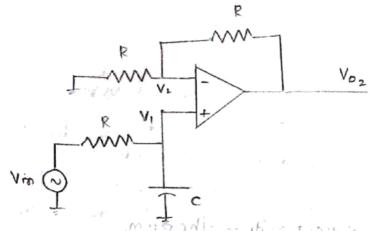

Applying Noltage divides rule at yourse Viet Vim (s) Vise mole and to and part into h

For negative feedback,

Applying the nodal analysis at investing terminal. $\frac{V_2 - 0}{R} + 4 = 0$ No2 = RV2 Vo2= 1+sck Vm(s) Total Response, Vo = Vo1+Vo2 = -Vin(s) + 2 . Vin(s) Vincs) 1+scr 1+ scR In frequency domain, $\frac{V_{o}(f)}{V_{m}(f)} = \frac{1-j2\pi FC}{1+j2\pi FC}$ $\left| \frac{V_o(f)}{V_{in}(f)} \right| = \frac{\sqrt{1 + (2\pi F RC)^2}}{\sqrt{1 + (2\pi F RC)^2}}$ $A \rightarrow A = 1$ $\sqrt{\frac{V_0(f)}{V_m(f)}} = \tan^{-1}(-2\pi Rc) - \tan^{-1}(2\pi fRc)$ tan' (-0)= tan' (0) on 10 = ylam 10 both = - tan' (2xPRCY- tan' (2xPC)

 $f \rightarrow 0$ (d.c signal) $\rightarrow \langle \frac{V_0(f)}{V_{in}(f)} = 0 \rangle$ $f \rightarrow \infty$ (a.c. signal) $\rightarrow \langle \frac{V_0(f)}{V_{in}(f)} = -180^\circ$

Section Services

alk Nobel

The gain magnitude is 1, i.e. independent of the frequency, so, output is equal to input But, a phose change exists between the input and Output based on the input signal frequency. It can generate - 180° to 0° phase shift between the output and input, i.e. input leads the output.

BAND PASS FILTER:


> Narrow Band Pass (B.Wisless) @>10 - Wide Band Pass (B.Wis more) Qc10

0 = fo = fo where fo = V finfe

1 B.W fh-fl centre frequency

473 F

NARROW BAND PASS FILTER

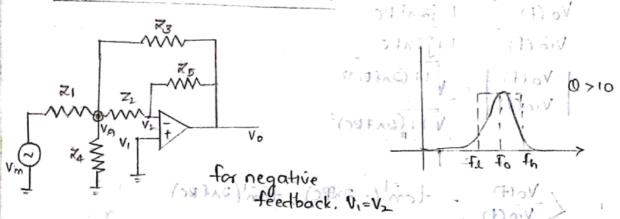

Nodal analysis at mode voltage VA. I mit

$$\frac{V_{A}-V_{in}}{\bowtie} + \frac{V_{A}-V_{2}}{\bowtie} + \frac{V_{A}+O_{C}}{\bowtie} + \frac{V_{A}-V_{0}}{\bowtie} = 0$$

$$3.4 \ V_{0}=0$$

But
$$V_2 = 0$$
,
 $V_A \left[\begin{array}{c} \frac{1}{2} + \frac{1}{2} + \frac{1}{2} + \frac{1}{2} + \frac{1}{2} + \frac{1}{2} \\ \frac{1}{2} + \frac{1}{2} + \frac{1}{2} + \frac{1}{2} + \frac{1}{2} \\ \frac{1}{2} + \frac{1}{2} + \frac{1}{2} + \frac{1}{2} + \frac{1}{2} \\ \frac{1}{2} + \frac{1}{2} \\ \frac{1}{2} + \frac{1}{2$

VA [Y1+ Y2+ Y3+ Y4] = Vin Y1 + Vo Y3 -> 1 Applying nodal analysis at inverting node, $\frac{V_2 - V_A}{Z_F} + \frac{V_2 - V_0}{Z_F} + 0 = 0$ But 12 = 010 1 13 30 - 31 22 1 30 1 1 23 2 23 $-V_{A}.Y_{2} = V_{0}Y_{5}$ $\begin{array}{c} V_{A} = -\frac{V_{5}}{V_{2}} \cdot V_{0} \rightarrow \textcircled{2} \\ \hline \end{array}$ from (1) and (2), $-\frac{y_5}{y_2} \cdot V_0 \left[y_1 + y_2 + y_3 + y_4 \right] = V_m y_1 + V_0 y_3$ $-V_{0}Y_{5}[Y_{1}+Y_{2}+Y_{3}+Y_{4}]=V_{in}(Y_{1}Y_{2})+V_{0}(Y_{3}Y_{2})$ - Vo [Y2 Y3 + Y5 (Y1+Y2+ Y3+Y4)] = Vin (Y1 Y2) Vo = - Y1 Y2 election to book projection of the T C3 (4) V + 13 R_1 C_2 V_0 V_0 Z= R1 Z=5C2 Z3 = 1/8C3 Z4= R4) Z5= R5000

Y1 = G1 Y2 = SC2 X3 = SC3 = X4 = G4 Y6 = G5 mold

$$\frac{V_0}{V_{in}} = \frac{-(G_1.6G_2)}{(8G_2)(8G_3) + G_5[G_1+8G_2+6G_3+G_4]}$$

8G. 8C3 + G1G5 + 5C2. G5 + G5.8C3 + G4 G5

Dividing with scz,

$$\frac{-G_1 \cdot SG_2}{SC_3 + G_5 \left[1 + \frac{C_3}{C_2}\right] + \frac{G_5}{SC_2} \left[G_1 + G_4\right]} \rightarrow \emptyset$$

RLC Parallel Circuit:


$$I + \frac{V_0(s)}{sL} + \frac{V_0(s)}{R} + \frac{V_0(s)}{V_{sc}} + 0 = 0$$

$$\frac{V\dot{m}}{Rin} + Vo(s) \left[\frac{1}{sL} + \frac{1}{R} + sc \right] + 0 = 0$$


$$\frac{V_{rin}}{R_{rin}} = -V_0(s) \left[\frac{1}{s1} + G + sc \right]$$

Quality factor. Q = R = WORC Bandwidth = fo [..., O= fo/B.w]. On companision with (B), (the transfer function of with (B), (the transfer function of RLC Parallel Circuit) We get. -(-transfer function of IVBPF) Gin= G1 G= G5 [1+ C3] G5 [G1+G4] Resonant frequency, wor The $\sqrt{\frac{C_2}{C_2 C_3}} = \sqrt{\frac{G_5 (G_1 + G_4)}{C_2 C_3}}$ Maximum Gam, Ao = Vo $= -\frac{G_{1}n}{G} = \frac{-G_{1}}{G_{5}\left[1 + \frac{C_{3}}{C_{5}}\right]} = \frac{-G_{1}C_{2}}{G_{5}\left(C_{2} + C_{3}\right)}$ Quality factor, 0 = R = 1 wo GL \[\begin{align*} \frac{G_5(G_1+G_4)}{G_5(G_1+G_4)} & \frac{G_5(G_1+G_4)}{G_5(G_1+G_4)} \end{align*} \] = 1 (9,+64) (93) Bandwidth, = fo wo 2x 10

WIDE BAND PASS FILTERS

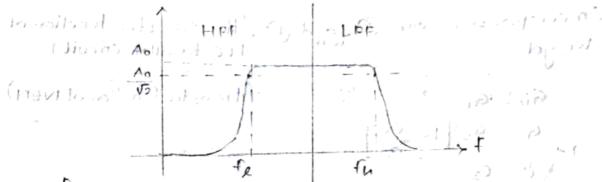

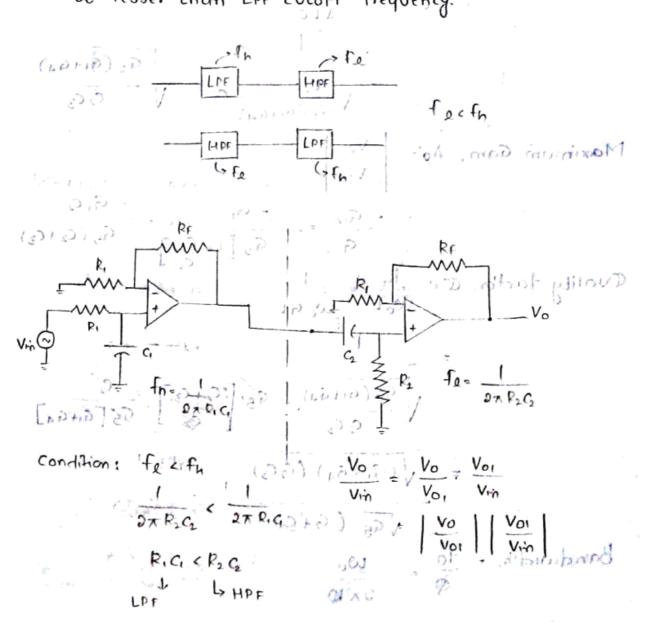By the cascade connection of LPH and HPF, we can design the band pass filter.
But the condition is HPF cutoff frequency (fl) should be lesser than LPF cutoff frequency.





$$\frac{V_0}{V_{in}} = \frac{V_0}{V_{01}} \cdot \frac{V_{01}}{V_{im}}$$

$$\frac{V_0}{V_{in}} = \frac{V_0}{V_{01}} \cdot \frac{V_{01}}{V_{01}} \cdot \frac{V_{01}}{V_{01}$$

BAND REJECT FILTER:

For Narrow BRF,

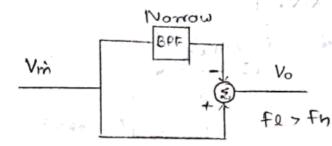

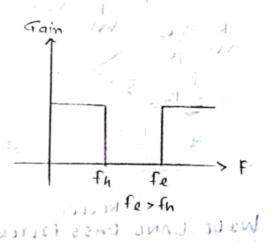

-for Nermo Wide BRF,

Vin

Fe

HPF

HPF


L> cutoff frequof HPF

Narrow Band Reject filter:

for this fe>fh, but fe is closer to fh. To design this, we are using the Band pass filter, i.e, by subtracting the band pass filter output from the input, we can clesign the band reject filter.

But in this, the maximum gain of Band Pass filter should be 1.

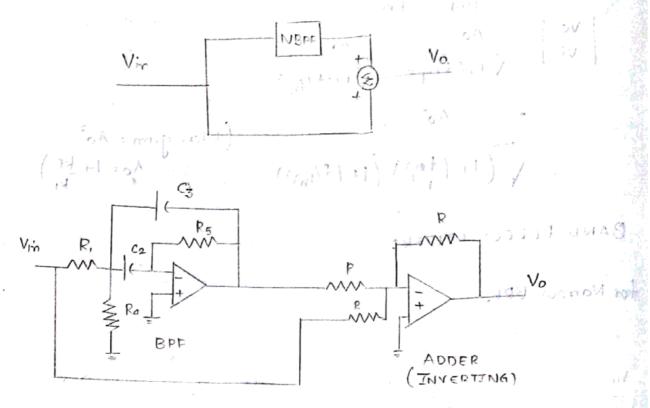But NBF filter output is negative (Gain). So, instead of subtracting from the input, we are adding the NBF output to the input.



WIDE BAND PASS FILTER:

In this fe >>fh,

By adding of the outputs of LPF and PAPF. We can get the output of Wide Band Pass filter.

1718 shill one of

